

计算机组成原理 实验报告

实验题目：流水线CPU设计

学生姓名：阿非提

学生学号：PB20111633

完成日期：2022.5.18

实验目的

- 理解流水线CPU的结构和工作原理
- 掌握流水线CPU的设计和调试方法，特别是流水线中数据相关和控制相关的处理
- 熟练掌握数据通路和控制器的设计和描述方法


实验平台

- Vivado
- Rars

实验练习

- cpu设计

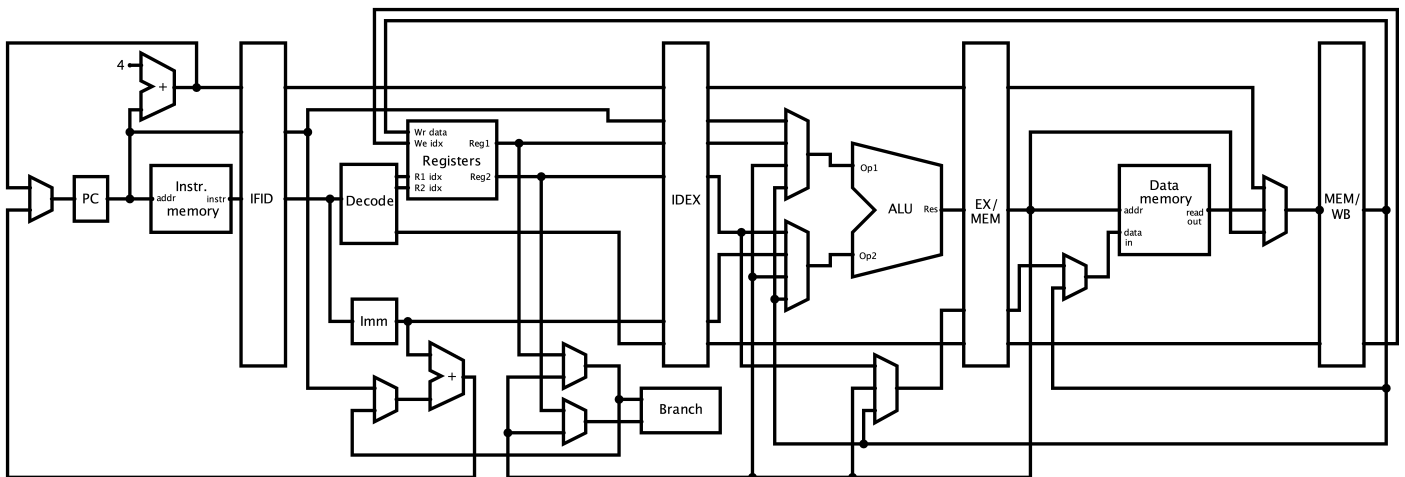在Ripes 提供的流水线处理器的数据通路的基础上，将控制冒险前移到 ID 阶段得到如下数据通路。



设计文件

寄存器堆

经过修改，寄存器堆会在写地址端口 `write_register` 不为零时进行写入操作。

```
module register_file(  
    input clk,rst,  
    input [4:0] read_register1,
```

```

input [4:0] read_register2,
input [4:0] write_register,
input [31:0] write_data,
output reg [31:0] read_data1,
output reg [31:0] read_data2,
//debug port
input [4:0] debug_register,
output reg [31:0] debug_register_data
);

reg [31:0] registers[0:31];
integer i;

always@(*)begin
    if(read_register1)begin
        if(read_register1 == write_register)
            read_data1 = write_data;
        else
            read_data1 = registers[read_register1];
    end
    else
        read_data1 = 0;
end

always@(*)begin
    if(read_register2)begin
        if(read_register2 == write_register)
            read_data2 = write_data;
        else
            read_data2 = registers[read_register2];
    end
    else
        read_data2 = 0;
end

always@(*)begin
    if(debug_register)begin
        if(debug_register == write_register)
            debug_register_data = write_data;
        else
            debug_register_data = registers[debug_register];
    end
    else
        debug_register_data = 0;
end

always@(posedge clk or posedge rst)begin
    if(rst)

```

```

        for(i = 0; i < 32; i = i + 1)
            registers[i] <= 0;
    else if(write_register != 5'b0)
        registers[write_register] <= write_data;
    end

endmodule

```

alu

```

module alu(
    input [31:0] operand1,operand2,
    input [2:0] operation_code,
    output reg [31:0] result
);

    wire signed [31:0] signed_operand1 = operand1;
    wire signed [31:0] signed_operand2 = operand2;

    always@(*)begin
        case(operation_code)
            3'h0: result = signed_operand1 + signed_operand2;
            3'h1: result = signed_operand1 - signed_operand2;
            3'h2: result = signed_operand1 & signed_operand2;
            3'h3: result = signed_operand1 | signed_operand2;
            3'h4: result = signed_operand1 ^ signed_operand2;
            3'h5: result = signed_operand1 << signed_operand2;
            3'h6: result = signed_operand1 >> signed_operand2;
            default: result = 0;
        endcase
    end

endmodule

```

立即数扩展

```

module immediate_Generator(
    input [31:0] inst,
    output reg [31:0] imme
);
    always@(*)begin
        case(inst[6:0])
            7'b0000011: imme = {{21{inst[31]}},inst[30:20]};//I-type
            7'b0010011: imme = {{21{inst[31]}},inst[30:20]};//I-type
            7'b1100111: imme = {{21{inst[31]}},inst[30:20]};//I-type
            7'b0100111: imme = {{21{inst[31]}},inst[30:25],inst[11:7]};//S-type

```

```

        7'b1100011: imme = {{20{inst[31]}}},inst[7],inst[30:25],inst[11:8],1'b0};//SB-
type
        7'b1101111: imme = {{13{inst[31]}}},inst[19:12],inst[20],inst[30:21],1'b0};//
UJ-type
        7'b0010111: imme = {inst[31:12],12'h0};//U-type
        default: imme = 32'h0;
        endcase
end

```

endmodule

pc

```

module PC(
    input clk,rst,en,
    input [31:0] pc_input,
    output reg [31:0] pc
);

    always@(posedge clk or posedge rst)begin
        if(rst)
            pc <= 32'h00003000;
        else if(en)
            pc <= pc_input;
    end
endmodule

```

decode

```

module decode(
    input [31:0] instruction,
    output [4:0] reg_addr1,
    output [4:0] reg_addr2,
    output [4:0] reg_write_addr,
    output reg [1:0] reg_write_sel,
    output mem_write,
    output reg [1:0] alu_a_sel,
    output reg [1:0] alu_b_sel,
    output reg [2:0] alu_opcode,
    output is_r1_ID_needed,
    output is_r2_ID_needed,
    output is_r1_EX_needed,
    output is_r2_EX_needed,
    output is_r2_MEM_needed,
    output is_jal,
    output is_jalr,
    output is_branch,
    output reg [1:0] branch_type
);

```

```

assign reg_addr1 = instruction[19:15];
assign reg_addr2 = instruction[24:20];

wire [6:0] opcode = instruction[6:0];
wire [6:0] funct7 = instruction[31:25];
wire [2:0] funct3 = instruction[14:12];

wire is_add = (opcode == 7'b0110011) && (funct3 == 3'b000) && (funct7 == 7'b0000000);
wire is_addi = (opcode == 7'b0010011) && (funct3 == 3'b000);
wire is_sub = (opcode == 7'b0110011) && (funct3 == 3'b000) && (funct7 == 7'b0100000);
wire is_and = (opcode == 7'b0110011) && (funct3 == 3'b111) && (funct7 == 7'b0000000);
wire is_andi = (opcode == 7'b0010011) && (funct3 == 3'b111);
wire is_or = (opcode == 7'b0110011) && (funct3 == 3'b110) && (funct7 == 7'b0000000);
wire is_ori = (opcode == 7'b0010011) && (funct3 == 3'b110);
wire is_xor = (opcode == 7'b0110011) && (funct3 == 3'b100) && (funct7 == 7'b0000000);
wire is_xori = (opcode == 7'b0010011) && (funct3 == 3'b100);
wire is_sll = (opcode == 7'b0110011) && (funct3 == 3'b001) && (funct7 == 7'b0000000);
wire is_slli = (opcode == 7'b0010011) && (funct3 == 3'b001) && (funct7 == 7'b0000000);
wire is_srl = (opcode == 7'b0110011) && (funct3 == 3'b101) && (funct7 == 7'b0000000);
wire is_srli = (opcode == 7'b0010011) && (funct3 == 3'b101) && (funct7 == 7'b0000000);
wire is_auipc = (opcode == 7'b0010111);
wire is_beq = (opcode == 7'b1100011) && (funct3 == 3'b000);
wire is_bne = (opcode == 7'b1100011) && (funct3 == 3'b001);
wire is_blt = (opcode == 7'b1100011) && (funct3 == 3'b100);
wire is_bge = (opcode == 7'b1100011) && (funct3 == 3'b101);
assign is_jal = (opcode == 7'b1101111);
assign is_jalr = (opcode == 7'b1100111);
wire is_lw = (opcode == 7'b0000011) && (funct3 == 3'b010);
wire is_sw = (opcode == 7'b0100011) && (funct3 == 3'b010);
wire is_regWrite = is_add | is_addi | is_sub | is_and | is_andi | is_or | is_ori | is_xor | is_xori | is_sll | is_slli | is_srl | is_srli | is_auipc | is_jal | is_jalr | is_lw;
assign is_branch = is_beq | is_bge | is_blt | is_bne;
wire is_imm = is_addi | is_andi | is_ori | is_xori | is_slli | is_srli | is_auipc | is_sw | is_lw;
assign mem_write = is_sw;
assign reg_write_addr = is_regWrite ? instruction[11:7] : 5'h0;
assign is_r1_ID_needed = is_beq | is_bge | is_blt | is_bne | is_jalr;
assign is_r2_ID_needed = is_beq | is_bge | is_blt | is_bne;

```

```

    assign is_r1_EX_needed = is_add | is_addi | is_sub | is_and | is_andi | is_or
| is_ori | is_xor | is_xori | is_sll | is_slli | is_srl | is_srli | is_lw |
is_sw;
    assign is_r2_EX_needed = is_add | is_sub | is_and | is_or | is_xor |
is_sll | is_srl | is_sw;
    assign is_r2_MEM_needed = is_sw;

always@(*)begin
    if(is_beq)
        branch_type = 2'h0;
    else if(is_blt)
        branch_type = 2'h1;
    else if(is_bge)
        branch_type = 2'h2;
    else
        branch_type = 2'h3;
end

always@(*)begin
    if(is_jal | is_jalr)
        reg_write_sel = 2'h1;
    else if(is_lw)
        reg_write_sel = 2'h2;
    else
        reg_write_sel = 2'h0;
end

always@(*)begin
    if(is_auiopc)
        alu_a_sel = 2'h1;
    else
        alu_a_sel = 2'h0;
end

always@(*)begin
    if(is_imm)
        alu_b_sel = 2'h1;
    else
        alu_b_sel = 2'h0;
end

always@(*) begin
    if(is_add | is_addi)
        alu_opcode = 3'h0;
    else if(is_sub)
        alu_opcode = 3'h1;
    else if(is_and | is_andi)
        alu_opcode = 3'h2;
    else if(is_or | is_ori)
        alu_opcode = 3'h3;
    else if(is_xor | is_xori)
        alu_opcode = 3'h4;

```

```

        else if(is_sll | is_slli)
            alu_opcode = 3'h5;
        else if(is_srl | is_srli)
            alu_opcode = 3'h6;
        else
            alu_opcode = 0;
    end

endmodule

```

hazard

```

module hazerd_detection(
    input [4:0] ID_EX_reg_w_addr,
    input [4:0] EX_MEM_reg_w_addr,
    input [1:0] ID_EX_reg_write_sel,
    input [1:0] EX_MEM_reg_write_sel,
    input [4:0] reg_addr1,
    input [4:0] reg_addr2,
    input is_r1_ID_needed,
    input is_r2_ID_needed,
    input is_r1_EX_needed,
    input is_r2_EX_needed,
    input is_r2_MEM_needed,
    input [1:0] alu_a_sel,
    input [1:0] alu_b_sel,
    input is_branch,
    input is_jump,
    input branch_signal,
    input [31:0] reg_data1,
    input [31:0] reg_data2,
    input [31:0] EX_MEM_alu_result,
    output reg [1:0] ID_EX_alu_a_sel,
    output reg [1:0] ID_EX_alu_b_sel,
    output reg [1:0] ID_EX_sw_r2_sel,
    output [31:0] branch_input1,
    output [31:0] branch_input2,
    output [31:0] jalr_reg,
    output ID_EX_mem_write_sel,
    output stall,
    output flush
);

    wire is_r1_EX_dependent = (ID_EX_reg_w_addr != 0) && (reg_addr1 ==
ID_EX_reg_w_addr);
    wire is_r2_EX_dependent = (ID_EX_reg_w_addr != 0) && (reg_addr2 ==
ID_EX_reg_w_addr);

```

```

    wire is_r1_MEM_dependent = (EX_MEM_reg_w_addr != 0) && (reg_addr1 ==
EX_MEM_reg_w_addr);
    wire is_r2_MEM_dependent = (EX_MEM_reg_w_addr != 0) && (reg_addr2 ==
EX_MEM_reg_w_addr);
    wire ID_stall_by_EX = (is_r1_ID_needed && is_r1_EX_dependent) ||
(is_r2_ID_needed && is_r2_EX_dependent);
    wire ID_stall_by_MEM = ((is_r1_ID_needed && is_r1_MEM_dependent) ||
(is_r2_ID_needed && is_r2_MEM_dependent)) && (EX_MEM_reg_write_sel == 2'h2);
    wire EX_stall_by_MEM = ((is_r1_EX_needed && is_r1_EX_dependent) ||
(is_r2_EX_needed && is_r2_EX_dependent && (~is_r2_MEM_needed))) &&
(ID_EX_reg_write_sel == 2'h2);
    wire r1_ID_need_forward = is_r1_ID_needed && is_r1_MEM_dependent &&
(EX_MEM_reg_write_sel != 2'h2);
    wire r2_ID_need_forward = is_r2_ID_needed && is_r2_MEM_dependent &&
(EX_MEM_reg_write_sel != 2'h2);
    wire r1_EX_need_forward_EX_MEM = is_r1_EX_needed && is_r1_EX_dependent &&
(ID_EX_reg_write_sel != 2'h2);
    wire r2_EX_need_forward_EX_MEM = is_r2_EX_needed && is_r2_EX_dependent &&
(ID_EX_reg_write_sel != 2'h2);
    wire r1_EX_need_forward_MEM_WB = is_r1_EX_needed && is_r1_MEM_dependent;
    wire r2_EX_need_forward_MEM_WB = is_r2_EX_needed && is_r2_MEM_dependent;
    wire r2_MEM_need_forward = is_r2_MEM_needed && is_r2_EX_dependent &&
(ID_EX_reg_write_sel == 2'h2);
    assign stall = ID_stall_by_EX | ID_stall_by_MEM | EX_stall_by_MEM;
    assign flush = ~(ID_stall_by_EX | ID_stall_by_MEM ) & ((is_branch &
branch_signal) | is_jump);
    assign branch_input1 = r1_ID_need_forward ? EX_MEM_alu_result : reg_data1;
    assign branch_input2 = r2_ID_need_forward ? EX_MEM_alu_result : reg_data2;
    assign jalr_reg = r1_ID_need_forward ? EX_MEM_alu_result : reg_data1;
    assign ID_EX_mem_write_sel = r2_MEM_need_forward;

always@(*)begin
    if(r1_EX_need_forward_EX_MEM)
        ID_EX_alu_a_sel = 2'h2;
    else if(r1_EX_need_forward_MEM_WB)
        ID_EX_alu_a_sel = 2'h3;
    else
        ID_EX_alu_a_sel = alu_a_sel;
end

always@(*)begin
    if(~is_r2_MEM_needed & r2_EX_need_forward_EX_MEM)
        ID_EX_alu_b_sel = 2'h2;
    else if(~is_r2_MEM_needed & r2_EX_need_forward_MEM_WB)
        ID_EX_alu_b_sel = 2'h3;
    else
        ID_EX_alu_b_sel = alu_b_sel;
end

```



```

always@(*)begin
    if(r2_EX_need_forward_EX_MEM)
        ID_EX_sw_r2_sel <= 2'h1;
    else if(r2_EX_need_forward_MEM_WB)
        ID_EX_sw_r2_sel <= 2'h2;
    else
        ID_EX_sw_r2_sel <= 2'h0;
    end
endmodule

```

branch

```

module branch(
    input [1:0] branch_type, //0: beq, 1: blt
    input [31:0] input1,
    input [31:0] input2,
    output reg branch_signal
);
    wire signed [31:0] signed_input1 = input1;
    wire signed [31:0] signed_input2 = input2;

    always@(*)begin
        case(branch_type)
            2'h0:branch_signal = (signed_input1 == signed_input2)? 1:0;
            2'h1:branch_signal = (signed_input1 < signed_input2)? 1:0;
            2'h2:branch_signal = (signed_input1 >= signed_input2)? 1:0;
            2'h3:branch_signal = (signed_input1 != signed_input2)? 1:0;
            default::;
        endcase
    end
endmodule

```

data memory

```

module data_io_memory(
    input clk,
    input write_enable,
    input [31:0] addr,
    input [31:0] write_data,
    output [31:0] read_data,
    //io memory ports
    output io_we,
    output [7:0] io_addr,
    output [31:0] io_dout,
    input [31:0] io_din,
    //debug ports

```

```

input [7:0] m_rf_addr,
output [31:0] m_data
);

// is address in 0x0000_0000 ~ 0x0000_03ff range
wire is_data_ram = (addr[31:10] == 22'b0)? 1:0;

//if address is I/O memory address
assign io_we = (is_data_ram == 0)? write_enable : 0;
assign io_dout = write_data;
assign io_addr = addr[7:0];

//if address is memory address
wire data_ram_write = (is_data_ram == 1)? write_enable : 0;
wire [31:0] data_ram_data;

assign read_data = (is_data_ram == 1)? data_ram_data : io_din;

data_mem data_mem(
    .clk(clk),
    .a(addr[9:2]),
    .d(write_data),
    .we(data_ram_write),
    .spo(data_ram_data),
    //debug port
    .dpra(m_rf_addr),
    .dpo(m_data)
);

endmodule

```

cpu

```

module cpu(
    input clk,rst,
    //IO_BUS
    output [7:0] io_addr,
    output [31:0] io_dout,
    output io_we,
    input [31:0] io_din,
    //Debug_BUS
    input [7:0] m_rf_addr,
    output [31:0] rf_data,
    output [31:0] m_data,
    //PC/IF/ID register
    output [31:0] pc,
    output [31:0] pcd, //pc_id
    output [31:0] ir, //inst_id

```

```

    output [31:0] pcin,
    //ID/EX register
    output [31:0] pce, //pc_ex
    output [31:0] a,    //rf_rdata1_ex
    output [31:0] b,    //rf_rdata2_ex
    output [31:0] imm,
    output [4:0] rd,
    output [31:0] ctrl,
    output [31:0] y,
    output [31:0] bm,
    output [4:0] rdm,
    output [31:0] ctrlm,
    //MEM/WB register
    output reg [31:0] yw,
    output reg [31:0] mdr,
    output [4:0] rdw,
    output [31:0] ctrlw
);

//IF/ID registers
reg [31:0] IF_ID_pc;
reg [31:0] IF_ID_pc_plus4;
reg [31:0] IF_ID_instruction;

//ID/EX registers
reg [31:0] ID_EX_pc;
reg [31:0] ID_EX_pc_plus4;
reg [31:0] ID_EX_reg1;
reg [31:0] ID_EX_reg2;
reg [31:0] ID_EX_imm;
reg [4:0] ID_EX_reg_w_addr;
reg [1:0] ID_EX_reg_write_sel; // 0: alu result, 1: pc+4, 2: mem
reg [1:0] ID_EX_alu_a_sel; // 0: reg1, 1: pc, 2: EX/MEM, 3: MEM/WB
reg [1:0] ID_EX_alu_b_sel; // 0: reg2, 1: imm, 2: EX/MEM, 3: MEM/WB
reg [2:0] ID_EX_alu_opcode; //0: add, 1: sub, 2: and, 3: or, 4: xor, 5: shift
left, 6: shift right
reg ID_EX_mem_write_sel; //0: data, 1: MEM/WB
reg ID_EX_mem_write;
reg [1:0] ID_EX_sw_r2_sel;
wire stall;
wire flush;

//EX/MEM registers
reg [31:0] EX_MEM_pc_plus4;
reg [31:0] EX_MEM_alu_result;
reg [31:0] EX_MEM_data_mem_data;
reg [4:0] EX_MEM_reg_w_addr;
reg [1:0] EX_MEM_reg_write_sel; // 0: alu result, 1: pc+4, 2: mem

```

```

reg          EX_MEM_mem_write_sel; //0: data, 1: MEM/WB
reg          EX_MEM_mem_write;

//MEM/WB registers
reg [31:0] MEM_WB_reg_w_data;
reg [4:0] MEM_WB_reg_w_addr;

//IF stage

//pc
reg [31:0] pc_input;
PC PC(
    .clk(clk),
    .rst(rst),
    .en(~stall),
    .pc_input(pc_input),
    .pc(pc)
);

//instruction memory
wire [31:0] instruction;
instruction_mem instruction_mem(
    .a(pc[9:2]),
    .spo(instruction)
);

always@(posedge clk or posedge rst)begin
    if(rst | flush)begin
        IF_ID_pc <= 0;
        IF_ID_pc_plus4 <= 0;
        IF_ID_instruction <= 0;
    end
    else if(~stall)begin
        IF_ID_pc <= pc;
        IF_ID_pc_plus4 <= pc + 4;
        IF_ID_instruction <= instruction;
    end
end

//ID stage

//register file
wire [4:0] reg_addr1;
wire [4:0] reg_addr2;
wire [31:0] reg_data1;
wire [31:0] reg_data2;
register_file register_file(
    .clk(clk),

```

```

        .rst(rst),
        .read_register1(reg_addr1),
        .read_register2(reg_addr2),
        .write_register(MEM_WB_reg_w_addr),
        .write_data(MEM_WB_reg_w_data),
        .read_data1(reg_data1),
        .read_data2(reg_data2),
        .debug_register(m_rf_addr[4:0]),
        .debug_register_data(rf_data)
    );

//imm
wire [31:0] Imm;
imme imme(.inst(IF_ID_instruction),.imme(Imm));

//branch
wire [1:0] branch_type;
wire [31:0] branch_input1;
wire [31:0] branch_input2;
wire branch_signal;
branch branch(
    .branch_type(branch_type),
    .input1(branch_input1),
    .input2(branch_input2),
    .branch_signal(branch_signal)
);

//decode
wire [4:0] reg_write_addr;
wire [1:0] reg_write_sel;
wire mem_write;
wire [1:0] alu_a_sel;
wire [1:0] alu_b_sel;
wire [2:0] alu_opcode;
wire is_r1_ID_needed;
wire is_r2_ID_needed;
wire is_r1_EX_needed;
wire is_r2_EX_needed;
wire is_r2_MEM_needed;
wire is_jal;
wire is_jalr;
wire is_branch;

decode decode(
    .instruction(IF_ID_instruction),
    .reg_addr1(reg_addr1),
    .reg_addr2(reg_addr2),
    .reg_write_addr(reg_write_addr),
    .reg_write_sel(reg_write_sel),

```

```

        .mem_write(mem_write),
        .alu_a_sel(alu_a_sel),
        .alu_b_sel(alu_b_sel),
        .alu_opcode(alu_opcode),
        .is_r1_ID_needed(is_r1_ID_needed),
        .is_r2_ID_needed(is_r2_ID_needed),
        .is_r1_EX_needed(is_r1_EX_needed),
        .is_r2_EX_needed(is_r2_EX_needed),
        .is_r2_MEM_needed(is_r2_MEM_needed),
        .is_jal(is_jal),
        .is_jalr(is_jalr),
        .is_branch(is_branch),
        .branch_type(branch_type)
    );

//hazards detection
wire [1:0] id_ex_alu_a_sel;
wire [1:0] id_ex_alu_b_sel;
wire [1:0] id_ex_sw_r2_sel;
wire id_ex_mem_write_sel;
wire [31:0] jalr_reg;
hazard_detection hazard_detection(
    .ID_EX_reg_w_addr(ID_EX_reg_w_addr),
    .EX_MEM_reg_w_addr(EX_MEM_reg_w_addr),
    .ID_EX_reg_write_sel(ID_EX_reg_write_sel),
    .EX_MEM_reg_write_sel(EX_MEM_reg_write_sel),
    .reg_addr1(reg_addr1),
    .reg_addr2(reg_addr2),
    .is_r1_ID_needed(is_r1_ID_needed),
    .is_r2_ID_needed(is_r2_ID_needed),
    .is_r1_EX_needed(is_r1_EX_needed),
    .is_r2_EX_needed(is_r2_EX_needed),
    .is_r2_MEM_needed(is_r2_MEM_needed),
    .alu_a_sel(alu_a_sel),
    .alu_b_sel(alu_b_sel),
    .is_branch(is_branch),
    .is_jump(is_jal | is_jalr),
    .branch_signal(branch_signal),
    .reg_data1(reg_data1),
    .reg_data2(reg_data2),
    .EX_MEM_alu_result(EX_MEM_alu_result),
    .ID_EX_alu_a_sel(id_ex_alu_a_sel),
    .ID_EX_alu_b_sel(id_ex_alu_b_sel),
    .ID_EX_sw_r2_sel(id_ex_sw_r2_sel),
    .branch_input1(branch_input1),
    .branch_input2(branch_input2),
    .jalr_reg(jalr_reg),
    .ID_EX_mem_write_sel(id_ex_mem_write_sel),
    .stall(stall),

```

```

        .flush(flush)
    );

//pc

always@(*)begin
    if((is_branch & branch_signal) | is_jal)
        pc_input = IF_ID_pc + Imm;
    else if(is_jalr)
        pc_input = jalr_reg + Imm;
    else
        pc_input = pc + 4;
end

//ID->EX
always@(posedge clk or posedge rst)begin
    if(rst | stall)begin
        ID_EX_pc <= 0;
        ID_EX_pc_plus4 <= 0;
        ID_EX_reg1 <= 0;
        ID_EX_reg2 <= 0;
        ID_EX_imm <= 0;
        ID_EX_reg_w_addr <= 0;
        ID_EX_reg_write_sel <= 0;
        ID_EX_alu_a_sel <= 0;
        ID_EX_alu_b_sel <= 0;
        ID_EX_alu_opcode <= 0;
        ID_EX_mem_write_sel <= 0;
        ID_EX_mem_write <= 0;
        ID_EX_sw_r2_sel <= 0;
    end
    else begin
        ID_EX_pc <= IF_ID_pc;
        ID_EX_pc_plus4 <= IF_ID_pc_plus4;
        ID_EX_reg1 <= reg_data1;
        ID_EX_reg2 <= reg_data2;
        ID_EX_imm <= Imm;
        ID_EX_reg_w_addr <= reg_write_addr;
        ID_EX_reg_write_sel <= reg_write_sel;
        ID_EX_alu_a_sel <= id_ex_alu_a_sel;
        ID_EX_alu_b_sel <= id_ex_alu_b_sel;
        ID_EX_alu_opcode <= alu_opcode;
        ID_EX_mem_write_sel <= id_ex_mem_write_sel;
        ID_EX_mem_write <= mem_write;
        ID_EX_sw_r2_sel <= id_ex_sw_r2_sel;
    end
end

//EX stage

```

```

//alu
reg [31:0] operand1;
reg [31:0] operand2;
wire [31:0] alu_result;
alu alu(
    .operand1(operand1),
    .operand2(operand2),
    .operation_code(ID_EX_alu_opcode),
    .result(alu_result)
);

always@(*)begin
    case(ID_EX_alu_a_sel)
        2'h0:operand1 = ID_EX_reg1;
        2'h1:operand1 = ID_EX_pc;
        2'h2:operand1 = EX_MEM_alu_result;
        2'h3:operand1 = MEM_WB_reg_w_data;
    endcase
end

always@(*)begin
    case(ID_EX_alu_b_sel)
        2'h0:operand2 = ID_EX_reg2;
        2'h1:operand2 = ID_EX_imm;
        2'h2:operand2 = EX_MEM_alu_result;
        2'h3:operand2 = MEM_WB_reg_w_data;
    endcase
end

//EX->MEM
always@(posedge clk or posedge rst)begin
    if(rst)begin
        EX_MEM_pc_plus4 <= 0;
        EX_MEM_alu_result <= 0;
        EX_MEM_data_mem_data <= 0;
        EX_MEM_reg_w_addr <= 0;
        EX_MEM_reg_write_sel <= 0;
        EX_MEM_mem_write_sel <= 0;
        EX_MEM_mem_write <= 0;
    end
    else begin
        EX_MEM_pc_plus4 <= ID_EX_pc_plus4;
        EX_MEM_alu_result <= alu_result;
        case(ID_EX_sw_r2_sel)
            2'h0:EX_MEM_data_mem_data <= ID_EX_reg2;
            2'h1:EX_MEM_data_mem_data <= EX_MEM_alu_result;
            2'h2:EX_MEM_data_mem_data <= MEM_WB_reg_w_data;
        default;;
    end
end

```



```

        endcase
        EX_MEM_reg_w_addr <= ID_EX_reg_w_addr;
        EX_MEM_reg_write_sel <= ID_EX_reg_write_sel;
        EX_MEM_mem_write_sel <= ID_EX_mem_write_sel;
        EX_MEM_mem_write <= ID_EX_mem_write;
    end
end

//MEM stage

//data memory
wire [31:0] write_data = EX_MEM_mem_write_sel ? MEM_WB_reg_w_data :
EX_MEM_data_mem_data;
wire [31:0] read_data;
data_io_memory data_io_memory(
    .clk(clk),
    .write_enable(EX_MEM_mem_write),
    .addr(EX_MEM_alu_result),
    .write_data(write_data),
    .read_data(read_data),
    .io_we(io_we),
    .io_addr(io_addr),
    .io_dout(io_dout),
    .io_din(io_din),
    .m_rf_addr(m_rf_addr),
    .m_data(m_data)
);

always@(posedge clk or posedge rst)begin
    if(rst)begin
        MEM_WB_reg_w_data <= 0;
        MEM_WB_reg_w_addr <= 0;
    end
    else begin
        case(EX_MEM_reg_write_sel)
            2'h0:MEM_WB_reg_w_data <= EX_MEM_alu_result;
            2'h1:MEM_WB_reg_w_data <= EX_MEM_pc_plus4;
            2'h2:MEM_WB_reg_w_data <= read_data;
            default:MEM_WB_reg_w_data <= 0;
        endcase
        MEM_WB_reg_w_addr <= EX_MEM_reg_w_addr;
    end
end

//output modules
assign pcd = IF_ID_pc;
assign ir = IF_ID_instruction;
assign pcin = pc_input;
assign pce = ID_EX_pc;

```

```

    assign a = ID_EX_reg1;
    assign b = ID_EX_reg2;
    assign imm = ID_EX_imm;
    assign rd = ID_EX_reg_w_addr;
    assign ctrl = {stall,stall,(~stall &
flush),flush,2'b0,ID_EX_alu_a_sel,2'b0,ID_EX_alu_b_sel,1'b0,(ID_EX_reg_w_addr !=
5'h0),ID_EX_reg_write_sel,2'b0,(ID_EX_reg_write_sel ==
2'h2),ID_EX_mem_write,2'b0,(is_jal | is_jalr),(is_branch &
branch_signal),2'b0,alu_a_sel[0],alu_b_sel[0],ID_EX_alu_opcode};
    assign y = EX_MEM_alu_result;
    assign bm = EX_MEM_mem_write_sel ? MEM_WB_reg_w_data : EX_MEM_data_mem_data;
    assign rdm = EX_MEM_reg_w_addr;
    assign ctrlm =
{26'b0,EX_MEM_reg_write_sel,2'b0,EX_MEM_mem_write,EX_MEM_mem_write_sel};
    always@(posedge clk or posedge rst)begin
        if(rst)begin
            yw <= 0;
            mdr <= 0;
        end
        else begin
            yw <= (EX_MEM_reg_write_sel == 2'h0) ? EX_MEM_alu_result :
EX_MEM_pc_plus4;
            mdr <= read_data;
        end
    end
    assign rdw = MEM_WB_reg_w_addr;
    assign ctrlw = {31'b0,(MEM_WB_reg_w_addr != 5'h0)};

endmodule

```

• cpu功能仿真

运行使用的汇编代码

```

.data
    data1: .word 0xd
    data2: .word 0x3000
.text
    lw t1,data1      #t1 = 0xd
    addi t2,t1,0      #t2 = 0xd    //EX data hazards stalling
    add t3,t2,t1      #t3 = 0x1a   //EX data hazards forwarding from EX/MEM
    sub t4,t3,t2      #t4 = 0xd    //EX data hazards forwarding from MEM/WB

    beq t4,t2,Branch1 #branch taken //ID branch data hazards stalling and
forwarding from EX/MEM and flush

```

```

add t4,t4,t4

Branch1:lw t1,data2
jalr t1,t1,44      #t1 = 0x3028    //ID jump data hazards stalling and
forwarding from MEM/WB and flush

add t4,t4,t4
lw t1,data1
sw t1,4(zero).      #data2 = 0xd    //MEM data hazards forwarding

and t1,t4,t3        #t1 = 0x8
andi t1,t4,7        #t1 = 0x5
or t1,t4,t3         #t1 = 0x1f
ori t1,t4,2         #t1 = 0xf
xor t1,t4,t3        #t1 = 0x17
xori t1,t4,2        #t1 = 0xf
srli t1,t3,1        #t1 = 0xd
slli t1,t4,1        #t1 = 0x1a
addi t2,zero,1
srl t1,t3,t2        #t1 = 0xd
sll t1,t4,t2        #t1 = 0x1a
blt zero,t2,Branch2 #branch taken
add t4,t4,t4

Branch2:bge t2,zero,Branch3 #branch taken
add t4,t4,t4

Branch3:bne t2,zero,Branch4 #branch taken
add t4,t4,t4

Branch4:jal t1,Jump
add t4,t4,t4


Jump:

```


rars 生成的代码

Address	Code	Basic	Line	Source
0x00003000	0xffffd317	auipc x6,0xffffffff	5	lw t1,data1 #t1 = 0xd
0x00003004	0x00032303	lw x6,0(x6)	6	
0x00003008	0x00030303	addi x7,x6,0	7	addi t2,t1,0 #t2 = 0xd //EX data hazards stalling
0x0000300c	0x00639e33	add x28,x7,x6	8	add t3,t2,t1 #t3 = 0x1a //EX data hazards forwarding from EX/MEM
0x00003010	0x407e8eb3	sub x29,x28,x7	9	sub t4,t3,t2 #t4 = 0xd //EX data hazards forwarding from MEM/WB
0x00003014	0x007e8463	beq x29,x7,0x00000008	10	beq t4,t2,Branch1 #branch taken //ID branch data hazards stalling and forwarding from EX/MEM and flush
0x00003018	0x01de8eb3	add x29,x29,x29	11	add t4,t4,t4
0x0000301c	0xffffd317	auipc x6,0xffffffff	12	Branch1:lw t1,data2
0x00003020	0xfe832303	lw x6,0xffffffe8(x6)	13	
0x00003024	0x02c30367	jalr x6,x6,0x0000002c	14	jalr t1,t1,44 #jump //ID jump data hazards stalling and forwarding from MEM/WB and flush
0x00003028	0x01de8eb3	add x29,x29,x29	15	add t4,t4,t4
0x0000302c	0xffffd317	auipc x6,0xffffffff	16	lw t1,data1
0x00003030	0xfd432303	lw x6,0xfffffd4(x6)	17	
0x00003034	0x00602223	sw x6,4(x0)	18	sw t1,4(zero) #data2 = 0xd //MEM data hazards forwarding
0x00003038	0x01cef333	and x6,x29,x28	19	and t1,t4,t3 #t1 = 0x8
0x0000303c	0x007ef313	andi x6,x29,7	20	andi t1,t4,7 #t1 = 0x5
0x00003040	0x01cee333	or x6,x29,x28	21	or t1,t4,t3 #t1 = 0x1f
0x00003044	0x002ee313	ori x6,x29,2	22	ori t1,t4,2 #t1 = 0xf
0x00003048	0x01cec333	xor x6,x29,x28	23	xor t1,t4,t3 #t1 = 0x17
0x0000304c	0x002ec313	xori x6,x29,2	24	xori t1,t4,2 #t1 = 0xf
0x00003050	0x001e5313	srli x6,x28,1	25	srli t1,t3,1 #t1 = 0xd
0x00003054	0x001e9313	slli x6,x29,1	26	slli t1,t4,1 #t1 = 0x1a
0x00003058	0x00100393	addi x7,x0,1	27	addi t2,zero,1
0x0000305c	0x007e5313	srl x6,x28,x7	28	srl t1,t3,t2 #t1 = 0xd
0x00003060	0x007e9333	slli x6,x29,x7	29	sll t1,t4,t2 #t1 = 0x1a
0x00003064	0x00704463	blt x0,x7,0x00000008	30	blt zero,t2,Branch2 #branch taken
0x00003068	0x01de8eb3	add x29,x29,x29	31	add t4,t4,t4
0x0000306c	0x0003d463	bge x7,x0,0x00000008	32	Branch2:bge t2,zero,Branch3 #branch taken
0x00003070	0x01de8eb3	add x29,x29,x29	33	add t4,t4,t4
0x00003074	0x00039463	bne x7,x0,0x00000008	34	Branch3:bne t2,zero,Branch4 #branch taken
0x00003078	0x01de8eb3	add x29,x29,x29		add t4,t4,t4
0x0000307c	0x0080036f	jal x6,0x00000008		Branch4:jal t1,Jump
0x00003080	0x01de8eb3	add x29,x29,x29		add t4,t4,t4

流水线执行图

 

仿真结果

 

- 测试I/O版斐波拉契数列

测试代码由群文件提供。

设计文件（其中pdu为群文件提供的模块）

```
module top(  
    input clk,rst,        //clk,sw7  
    input run,            //sw6  
    input step,           //button  
    input valid,          //sw5  
    input [4:0] in,       //sw4-0  
    output [1:0] check,   //led6-5  
    output [4:0] out0,    //led4-0  
    output [2:0] an,      //an  
    output [3:0] seg,     //seg  
    output ready          //led7  
);
```

```
wire cpu_clk;  
wire [7:0] io_addr;  
wire [31:0] io_dout;  
wire io_we;  
wire [31:0] io_din;  
wire [7:0] m_rf_addr;  
wire [31:0] rf_data;  
wire [31:0] m_data;  
wire [31:0] pc;  
wire [31:0] pcd;  
wire [31:0] ir;  
wire [31:0] pcin;  
wire [31:0] pce;  
wire [31:0] a;  
wire [31:0] b;  
wire [31:0] imm;  
wire [4:0] rd;  
wire [31:0] ctrl;  
wire [31:0] y;  
wire [31:0] bm;  
wire [4:0] rdm;  
wire [31:0] ctrlm;  
wire [31:0] yw;  
wire [31:0] mdr;  
wire [4:0] rdw;  
wire [31:0] ctrlw;
```

```
cpu cpu(
```

```

        .clk(cpu_clk),
        .rst(rst),
        .io_addr(io_addr),
        .io_dout(io_dout),
        .io_we(io_we),
        .io_din(io_din),
        .m_rf_addr(m_rf_addr),
        .rf_data(rf_data),
        .m_data(m_data),
        .pc(pc),
        .pcd(pcd),
        .ir(ir),
        .pcin(pcin),
        .pce(pce),
        .a(a),
        .b(b),
        .imm(imm),
        .rd(rd),
        .ctrl(ctrl),
        .y(y),
        .bm(bm),
        .rdm(rdm),
        .ctrlm(ctrlm),
        .yw(yw),
        .mdr(mdr),
        .rdw(rdw),
        .ctrlw(ctrlw)
    );

```

```

pdu pdu(
    .clk(clk),
    .rst(rst),
    .run(run),
    .step(step),
    .clk_cpu(cpu_clk),
    .valid(valid),
    .in(in),
    .check(check),
    .out0(out0),
    .an(an),
    .seg(seg),
    .ready(ready),
    .io_addr(io_addr),
    .io_dout(io_dout),
    .io_we(io_we),
    .io_din(io_din),
    .m_rf_addr(m_rf_addr),
    .rf_data(rf_data),
    .m_data(m_data),

```

```


.pc(pc),
.pcd(pcd),
.ir(ir),
.pcin(pcin),
.pce(pce),
.a(a),
.b(b),
.imm(imm),
.rd(rd),
.ctrl(ctrl),
.y(y),
.bm(bm),
.rdm(rdm),
.ctrlm(ctrlm),
.yw(yw),
.mdr(mdr),
.rdw(rdw),
.ctrlw(ctrlw)
);


endmodule

```



运行结果


(前两项分别输入1, 2)

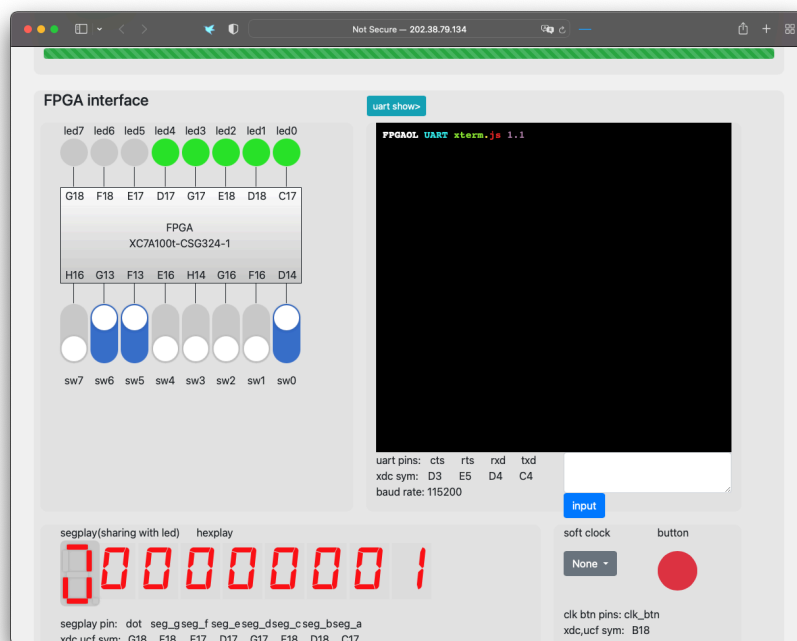

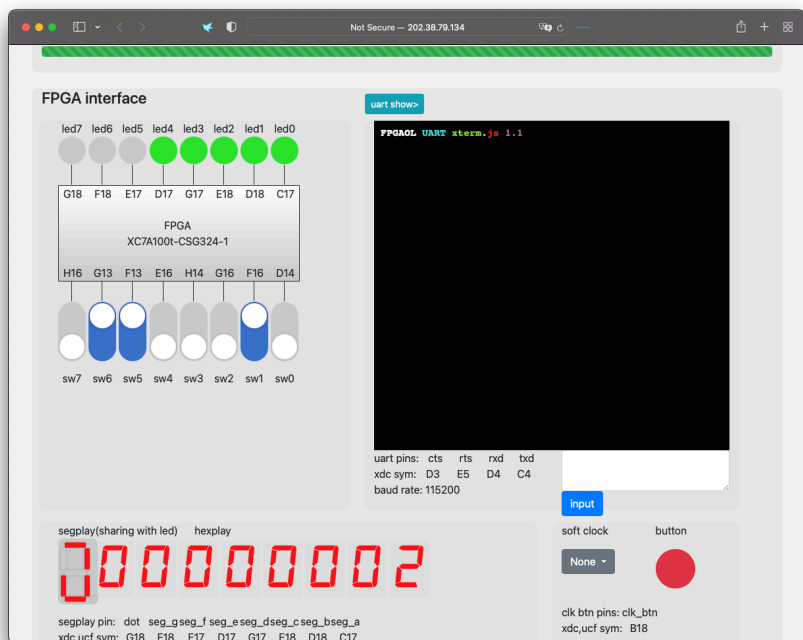

当停止运行时数据内存的状态

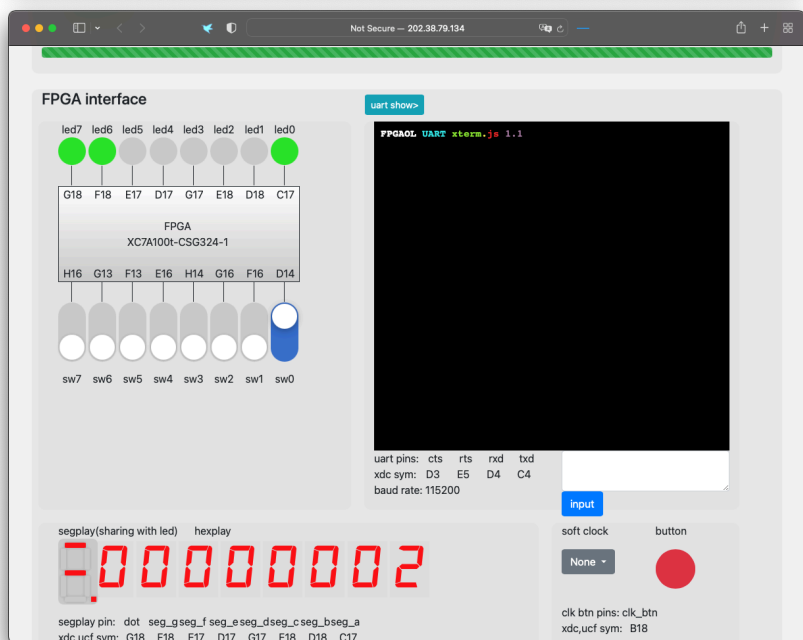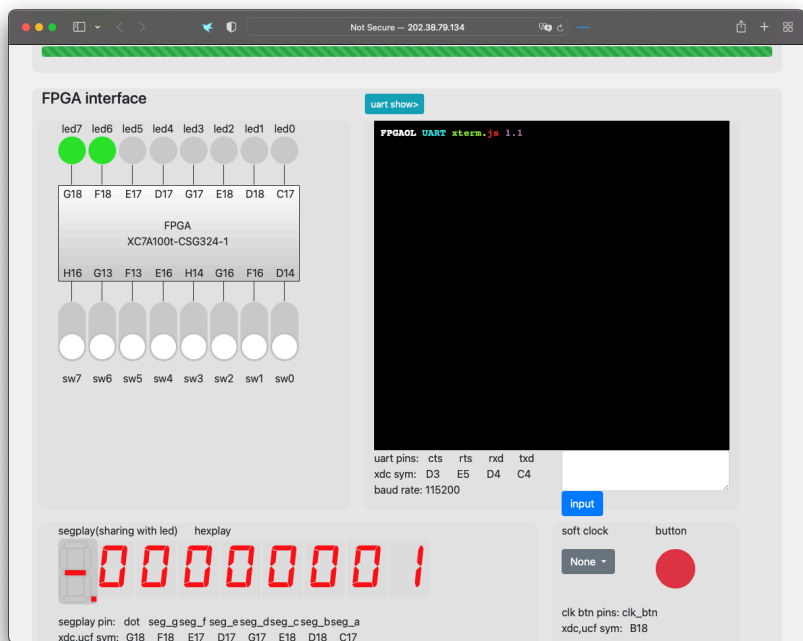

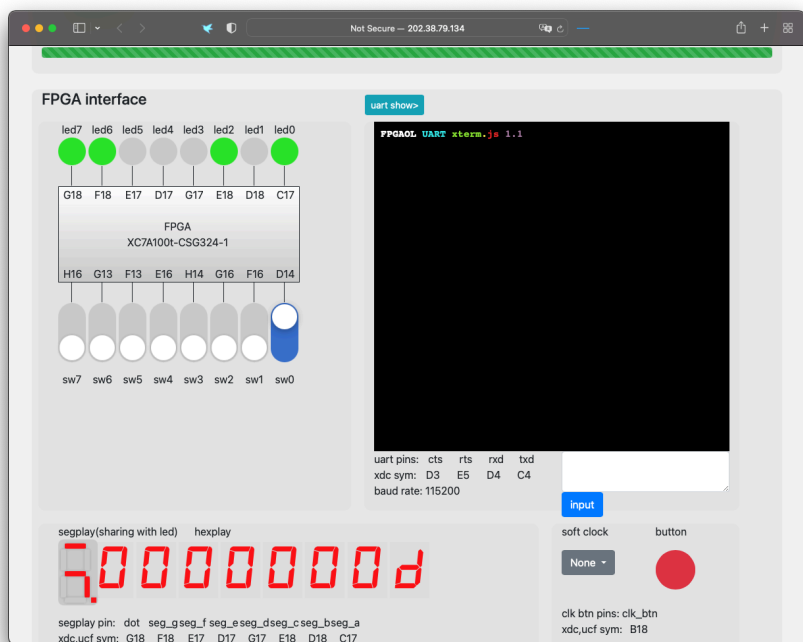

总结与思考

- 通过本次试验我更深入的了解了risc指令集下的流水线cpu的实现以及需要注意的事项。
- 本次试验难易程适中。
- 本次试验任务量适中。