

计算机组成原理 实验报告

实验题目：运算器及其原理

学生姓名：阿非提

学生学号：PB20111633

完成日期：2022.3.26

实验目的

- 掌握算术逻辑单元（ALU）功能
- 掌握数据通路和控制器的设计
- 掌握组合电路和时序电路，以及参数化和结构化的Verilog描述方法
- 了解查看电路性能和资源使用情况

实验平台

- Vivado

实验过程与结果

- 题目1


32位操作数计算逻辑单元

代码


```
module alu#(parameter WIDTH=32) (  
    input [WIDTH-1:0] a,b,  
    input [2:0] f,  
    output reg [WIDTH-1:0] y,  
    output z  
);  
  
    assign z=(y==0)?1:0;  
    always@(*)begin  
        case(f)  
            3'd0: y=a+b;  
            3'd1: y=a-b;  
            3'd2: y=a&b;  
            3'd3: y=a|b;  
            3'd4: y=a^b;  
            default::;  
        endcase  
    end
```

endmodule


RTL 电路

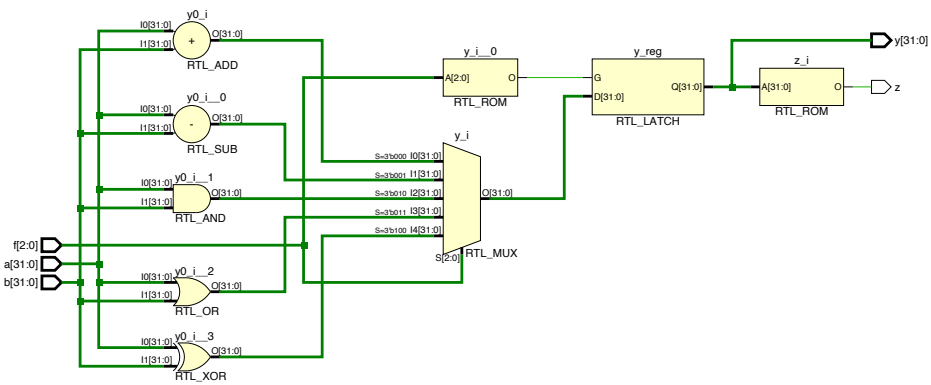

综合电路

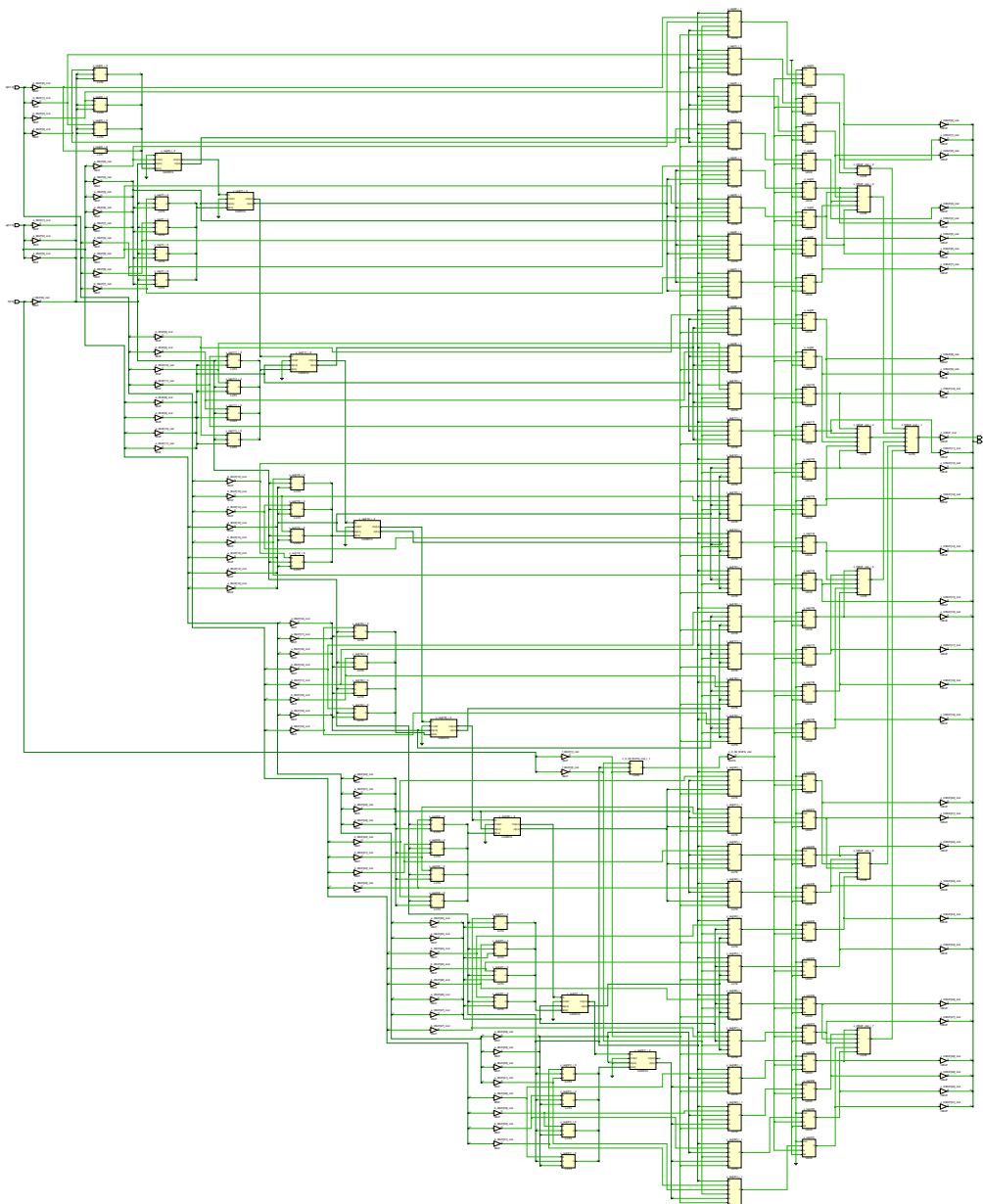


资源使用情况

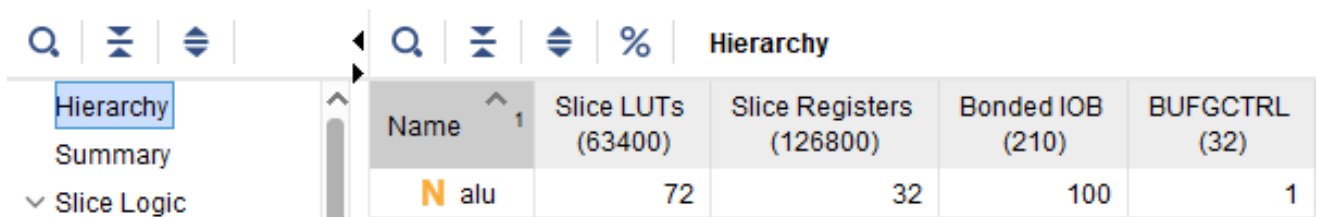

Name	Slice LUTs (63400)	Slice Registers (126800)	Bonded IOB (210)	BUFGCTRL (32)
alu	72	32	100	1

仿真结果

 

• 题目2

六位操作数算术逻辑单元

实例化上述ALU单元用于计算，用三个reg类型变量存储a, b, f的值。

代码

```
module ALU6bit(  
    input clk,  
    input en,  
    input [1:0] sel,  
    input [5:0] x,  
    output [5:0] y,  
    output z  
);  
reg [5:0] a,b;  
reg [2:0] f;  
alu #(6) alu(.a(a),.b(b),.f(f),.y(y),.z(z));  
always@(posedge clk)begin  
    if(en)begin  
        case(sel)  
            2'b00:a<=x;  
            2'b01:b<=x;  
            2'b10:f<=x[2:0];  
            2'b11:begin  
                a<=0;  
            end  
        endcase  
    end  
end
```


```

        b<=0;
        f<=0;


    end
    default::;
endcase
end
end
endmodule

```

RTL 电路

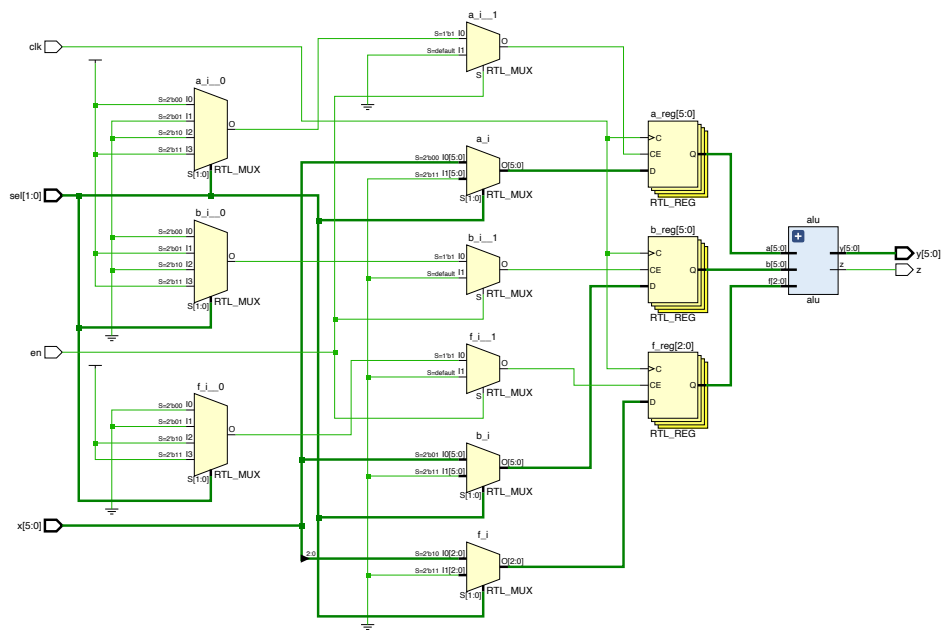

综合电路

 

				Hierarchy
Name	Slice LUTs (63400)	Slice Registers (126800)	Bonded IOB (210)	BUFGCTRL (32)
ALU6bit	20	15	17	1
alu (alu)	13	0	0	0


时间性能报告

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 8.730 ns	Worst Hold Slack (WHS): 0.147 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 3	Total Number of Endpoints: 3	Total Number of Endpoints: 16
All user specified timing constraints are met.		

Intra-Clock Paths - sys_clk_pin - Setup														
Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exception	Clock Un
Path 1	8.730	1	2	13	f_reg[0]/C	f_reg[0]/D	1.134	0.773	0.361	10.0	sys_clk_pin	sys_clk_pin		
Path 2	8.745	1	2	7	f_reg[1]/C	f_reg[1]/D	1.119	0.773	0.346	10.0	sys_clk_pin	sys_clk_pin		
Path 3	8.745	1	2	7	f_reg[2]/C	f_reg[2]/D	1.119	0.773	0.346	10.0	sys_clk_pin	sys_clk_pin		

仿真结果

 

运行结果

Bitstream File

Select file



example bitstream ▾

C:\fakepath\ALU6bit.bit

Program!

Program success!

FPGA interface

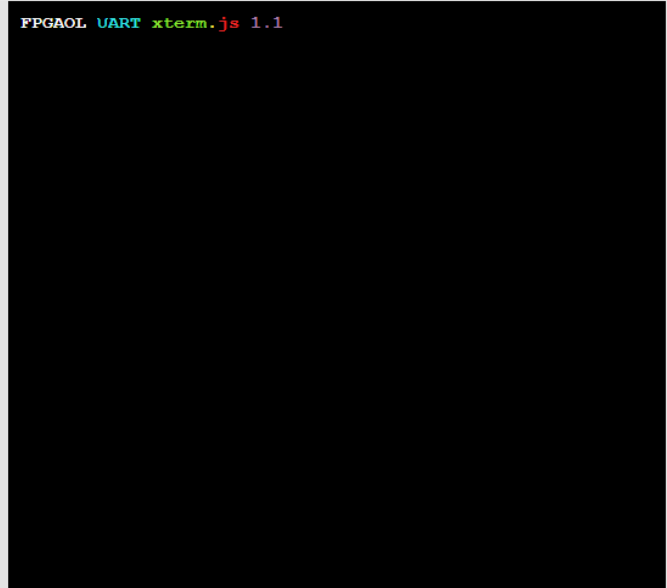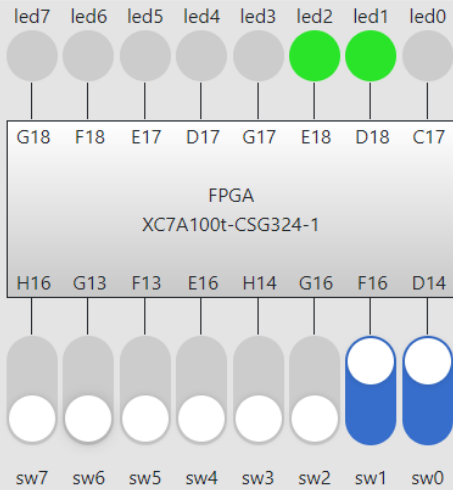

uart pins: cts rts rxd txd

segplay(sharing with led)

hexplay



segplay pin:	dot	seg_g	seg_f	seg_e	seg_d	seg_c	seg_b	seg_a
xdc,ucf sym:	G18	F18	E17	D17	G17	E18	D18	C17
hexplay pin:		an2	an1	an0	d3	d2	d1	d0
xdc,ucf sym:		A18	B16	B17	A15	A16	A13	A14

soft clock

button


None ▾

clk btn pins: clk_btn
xdc,ucf sym: B18

• 题目3

FLS

作出状态转化图

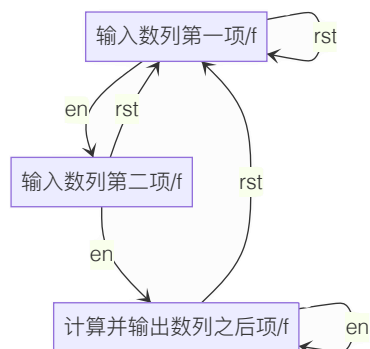

由此可知需要三种状态，分别记为state0、state1、state2。

由数列表达式可知 $F_n = F_{n-1} + F_{n-2}$ 可知，只需要两个变量存储当前项和前一项，分别记 f 、 f_0 。计算下一项只需 $f = f + f_0$ 。

需要注意的是 en 输入需要去除毛刺和取边缘。

代码

```
module FLS(
    input clk,rst,en,
    input [6:0] d,
    output reg [6:0] f
);

    reg [6:0] f0;
    wire [6:0] sum_of_f0_f;
    alu #(7) alu(.a(f0),.b(f),.f(0),.y(sum_of_f0_f));

    parameter state0 = 2'b00;
    parameter state1 = 2'b01;
    parameter state2 = 2'b10;
    parameter reset = 7'b0;

    reg [1:0] current_state;
    reg [1:0] next_state;

    //jitter cleaning
    reg [3:0] cnt;
    wire clean_button;
    always@(posedge clk)begin
        if(en==1'b0)cnt<=4'b0;
        else if(cnt<4'h8)cnt<=cnt+4'b1;
    end
    assign clean_button=cnt[3];

    //edge detection
    reg b1,b2;
    wire EN;

    always@(posedge clk)b1<=clean_button;
    always@(posedge clk)b2<=b1;
```



```

assign EN = b1&(~b2);

//NS
always@(*)begin
    if(EN)begin
        case(current_state)
            state0: next_state = state1;
            state1: next_state = state2;
            state2: next_state = state2;
            default;;
        endcase;
    end
    else next_state = current_state;
end

//CS
always@(posedge clk)begin
    if(rst)
        current_state <= state0;
    else
        current_state <= next_state;
end


//output
always@(posedge clk)begin
    if(rst)
        f <= 7'd0;
    else if(EN) begin
        case(current_state)
            state0: f <= d;
            state1: begin
                f0 <= f;
                f <= d;
            end
            state2: begin
                f0 <= f;
                f <= sum_of_f0_f;
            end
            default;;
        endcase
    end
end

```


end

endmodule

RTL电路

 

综合电路

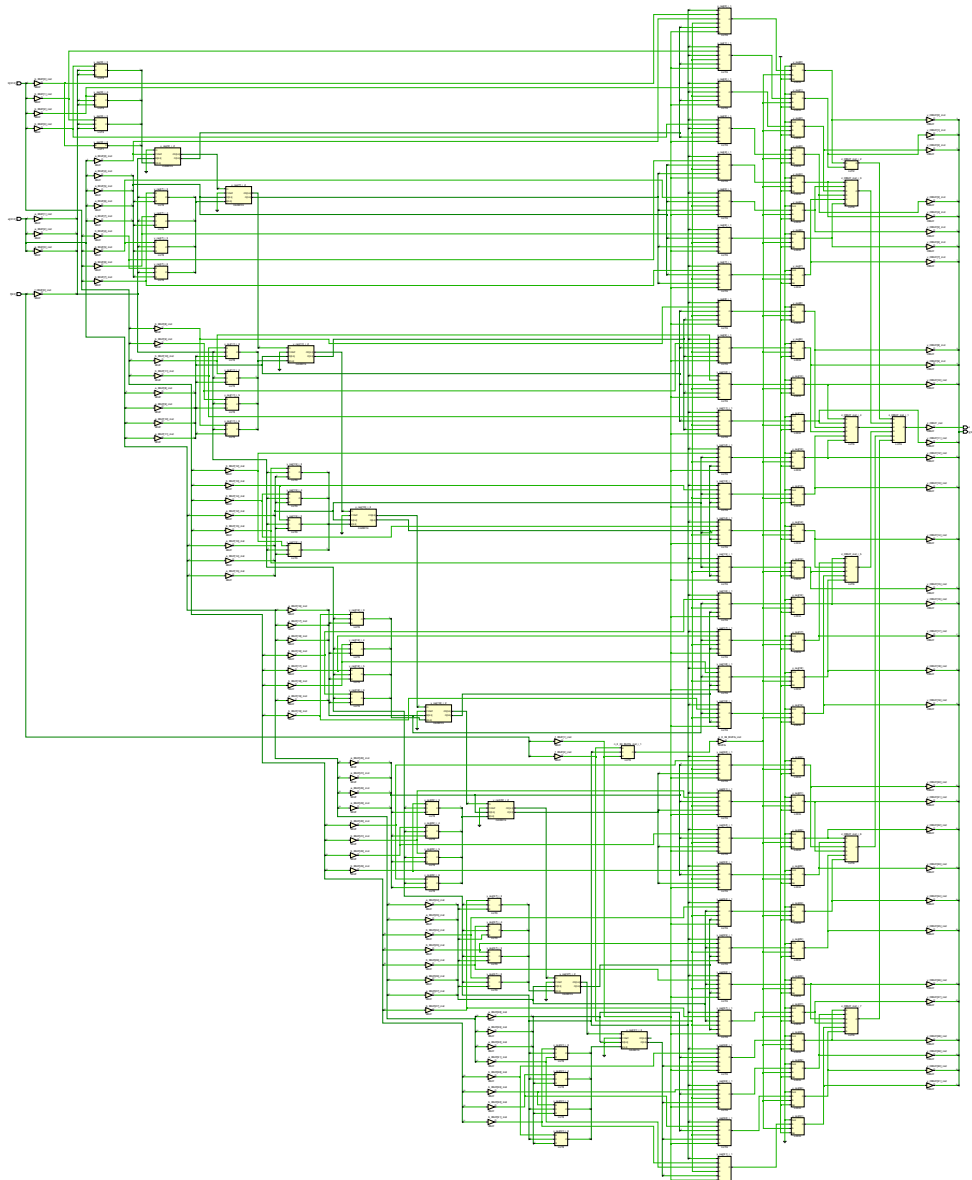

资源使用情况

Utilization				
Find Results				
Timing				
Hierarchy				
Name	Slice LUTs (63400)	Slice Registers (126800)	Bonded IOB (210)	BUFGCTRL (32)
FLS	20	24	17	1
alu (alu)	11	0	0	0

时间性能报告

Design Timing Summary

Setup

Worst Negative Slack (WNS): 7.063 ns
Total Negative Slack (TNS): 0.000 ns
Number of Failing Endpoints: 0
Total Number of Endpoints: 38

Hold

Worst Hold Slack (WHS): 0.137 ns
Total Hold Slack (THS): 0.000 ns
Number of Failing Endpoints: 0
Total Number of Endpoints: 38

Pulse Width


Worst Pulse Width Slack (WPWS): 4.500 ns
Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0
Total Number of Endpoints: 23

All user specified timing constraints are met.


Intra-Clock Paths - sys_clk_pin - Setup

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	Destination Clock	Exception	Clock Uncertainty
Path 1	7.063	4	5	4	f_reg[1]/C	f_reg[6]/D	2.801	1.855	0.946	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 2	7.109	4	5	4	f_reg[1]/C	f_reg[5]/D	2.755	1.949	0.806	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 3	7.199	3	4	4	f_reg[1]/C	f_reg[3]/D	2.665	1.723	0.942	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 4	7.234	4	5	4	f_reg[1]/C	f_reg[4]/D	2.630	1.825	0.805	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 5	7.274	3	4	4	f_reg[1]/C	f_reg[2]/D	2.590	1.644	0.946	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 6	7.503	1	2	7	current_state_reg[0]/C	f0_reg[0]/CE	2.115	0.773	1.342	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 7	7.503	1	2	7	current_state_reg[0]/C	f0_reg[1]/CE	2.115	0.773	1.342	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 8	7.503	1	2	7	current_state_reg[0]/C	f0_reg[2]/CE	2.115	0.773	1.342	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 9	7.503	1	2	7	current_state_reg[0]/C	f0_reg[3]/CE	2.115	0.773	1.342	10.0	sys_clk_pin	sys_clk_pin		0.035
Path 10	7.503	1	2	7	current_state_reg[0]/C	f0_reg[4]/CE	2.115	0.773	1.342	10.0	sys_clk_pin	sys_clk_pin		0.035

仿真结果

 

运行结果

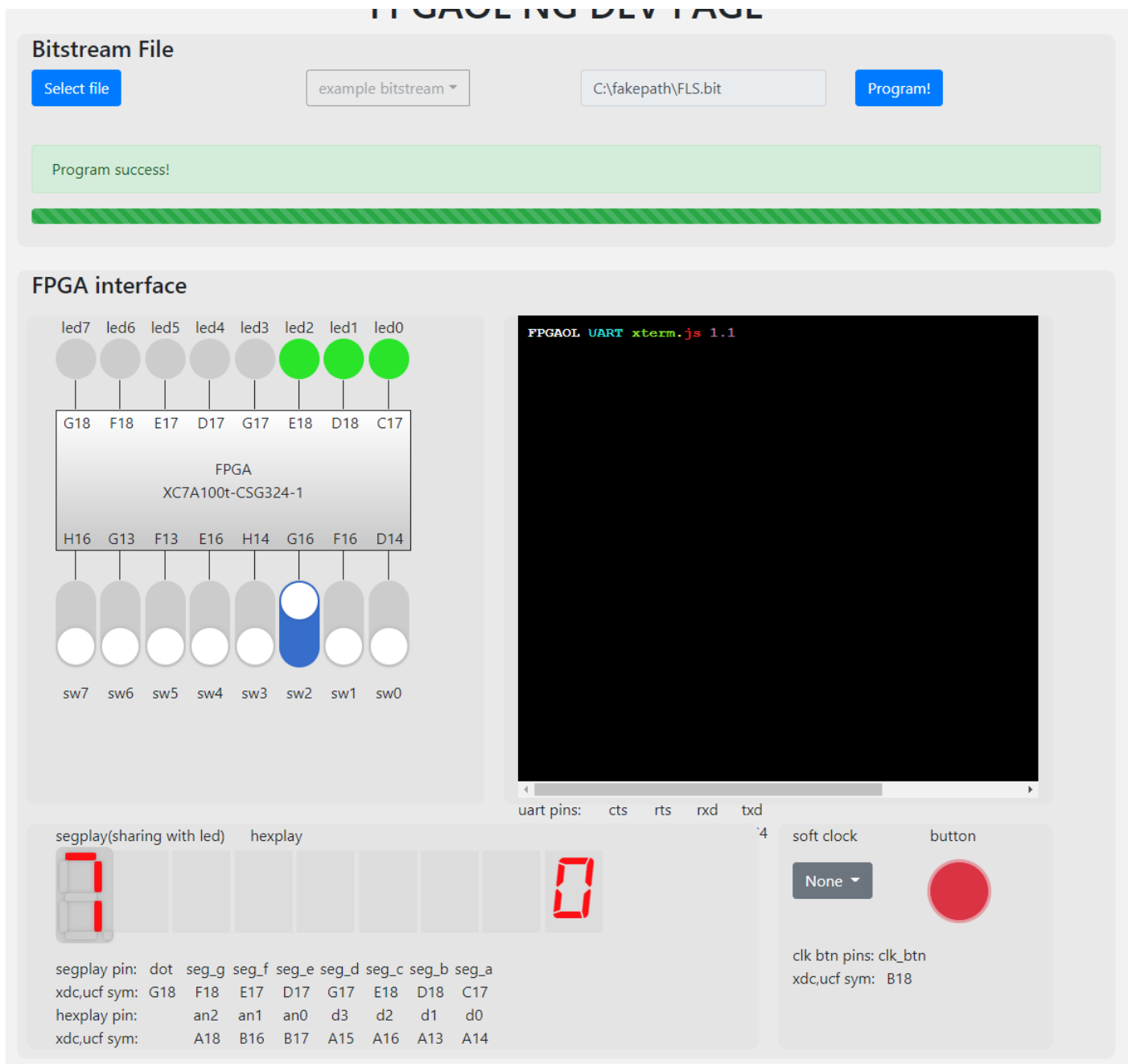

总结与思考

- 通过本次试验我学会了如何通过Vivado仿真工具进行Verilog 进行仿真，查看并分析波形文件。
- 本次试验难易程偏低。
- 本次试验任务量适中。